


24.05.2021

CS

IV Sem 'D'

Step response of first-order system:

Response Specifications for step input

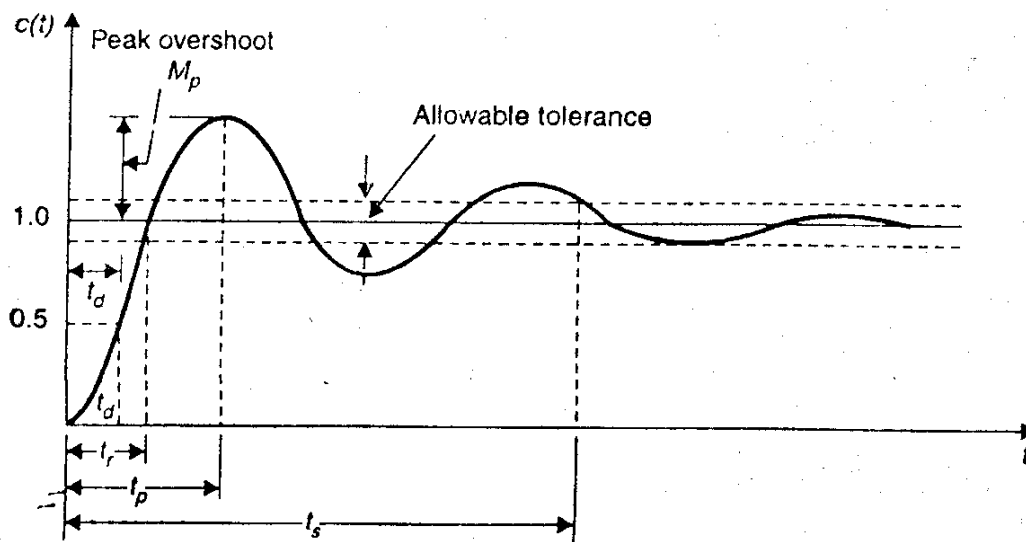

1. Delay time  $t_d$  : It is the time required for the response to reach 50% of its final value in first attempt.
2. Rise time  $t_r$  : It is the time required for the response to rise from 10% to 90% of its final value.


3 Peak time  $t_p$ : It is the time required for the response to reach its peak value.

4. peak overshoot  $M_p$ : It is the largest error b/w reference input and the output during the transient response

5. Settling time  $t_s$ : It is the time required for the response to settle or stay within a specified percentage (say  $\pm 2\%$  or  $\pm 5\%$ ) of its final value

Step response of first order system:

consider the circuit shown

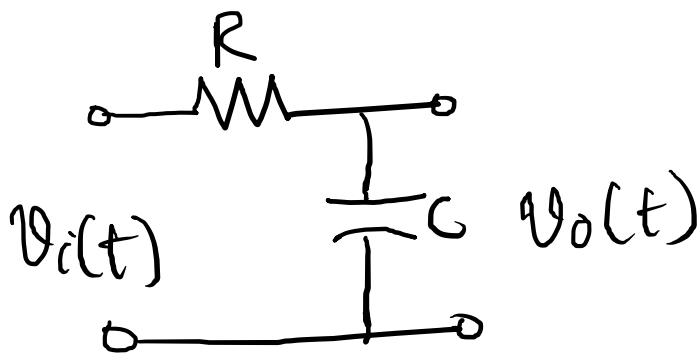

$$V_o(t) = \frac{1}{C} \int i \cdot dt \Rightarrow V_o(s) = \frac{I(s)}{Cs}$$

$$V_i(t) = iR + V_o(t) \Rightarrow V_i(s) = I(s)R + \frac{I(s)}{Cs}$$

let  $V_i(t)$  be  
step i/p

$$V_i(t) = 1; t \geq 0$$

$$V_i(t) = 0; t < 0$$

$$T.F = \frac{V_o(s)}{V_i(s)} = \frac{\frac{I(s)}{Cs}}{I(s)(R + \frac{1}{Cs})} = \frac{1}{RCs + 1}$$

$V_i(t) \rightarrow$  step i/p

$$\therefore V_i(s) = \frac{1}{s}$$

Pole at  
 $s = -\frac{1}{RC}$

$$V_o(s) = \frac{1}{RCs + 1} \times \frac{1}{s} = \frac{1}{s(RCs + 1)}$$

$$V_o(s) = \frac{A}{s} + \frac{B}{1 + RCs} \Rightarrow A = 1$$

$$B = -RC$$

$$\frac{1}{s} - \frac{RC}{1 + RCs} = \frac{1}{s} - \frac{1}{\frac{1}{RC} + s}$$

Taking Inverse Laplace Transform,

$$V_o(t) = 1 - e^{-t/RC}$$

$\rightarrow$  transient term is totally dependant on RC  
& Rate of exponential decay is controlled  
by  $-1/RC$ , which is pole of the system