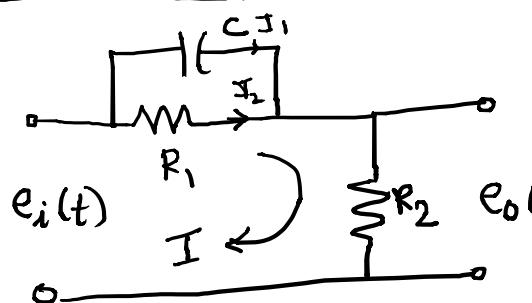


Transfer Functions of Lead and Lag Compensators:

Lead compensator:



$$I_1 + I_2 = I$$

$$C \frac{d}{dt} \frac{e_i(t) - e_o(t)}{R_2} + \frac{e_i(t) - e_o(t)}{R_1} = \frac{e_o(t)}{R_2}$$

$$\text{Taking L.T., } SC E_i(s) - SC E_o(s) + \frac{E_i(s)}{R_1} - \frac{E_o(s)}{R_1} = \frac{E_o(s)}{R_2}$$

$$E_i(s) \left[SC + \frac{1}{R_1} \right] = E_o(s) \left[SC + \frac{1}{R_1} + \frac{1}{R_2} \right]$$


$$\therefore T.F = \frac{E_o(s)}{E_i(s)} = \frac{SC + \frac{1}{R_1}}{SC + \frac{1}{R_1} + \frac{1}{R_2}} = \frac{C \left[S + \frac{1}{R_1 C} \right]}{C \left[S + \frac{1}{R_1 C} + \frac{1}{R_2 C} \right]}$$

$$T.F = \frac{S + \frac{1}{R_1 C}}{S + \frac{1}{R_1 C} + \frac{1}{R_2 C}} = \frac{S + \frac{1}{R_1 C}}{S + \frac{R_2 + R_1}{R_1 R_2 C}} = \frac{S + \frac{1}{R_1 C}}{S + \frac{1}{\left(\frac{R_2}{R_1 + R_2} \right) R_1 C}}$$

Let $T = R_1 C$ and $\frac{R_2}{R_1 + R_2} = \alpha$
 $\Rightarrow 0 < \alpha < 1$

$$T.F = \frac{S + \frac{1}{T}}{S + \frac{1}{\alpha T}} \rightarrow \text{This T.F is having a zero at } s = -\frac{1}{T} \text{ and a pole at } s = \frac{1}{\alpha T}$$

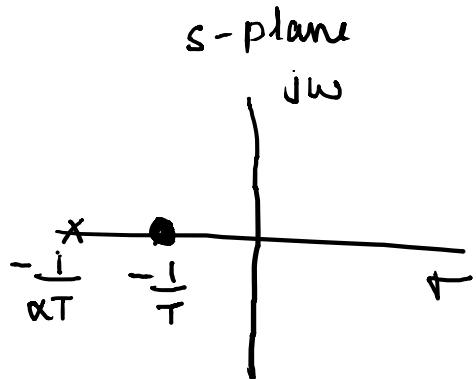\therefore Value of α lies b/w 0 & 1, pole always lies to the left of zero.



Effects of lead compensation


→ It adds a dominant zero and a pole
Thus ↑ the damping which results in less overshoot, small rise time and smaller settling time i.e., There is improvement in transient response

→ It also increases the Bandwidth of the system

Limitation

→ larger gain requirement

Lag compensator

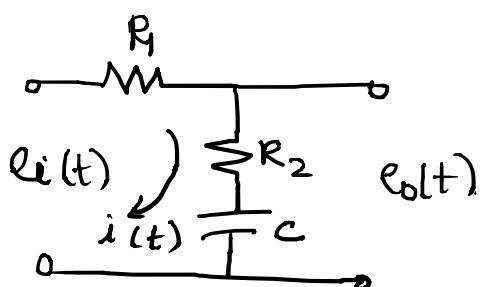

$$e_i(t) = i(t)R_1 + i(t)\frac{1}{C} \int i dt$$

Taking L.T

$$E_i(s) = I(s)R_1 + I(s)\frac{1}{C} + \frac{I(s)}{Cs}$$

$$E_i(s) = I(s) \left[R_1 + \frac{1}{C} + \frac{1}{Cs} \right]$$

The op equation is

$$e_o(t) = i(t)R_2 + \frac{1}{C} \int i dt$$

$$\text{Taking L.T, } E_o(s) = I(s) \left[R_2 + \frac{1}{Cs} \right]$$


$$\therefore T.F = \frac{E_o(s)}{E_i(s)} = \frac{R_2 + \frac{1}{Cs}}{R_1 + R_2 + \frac{1}{Cs}} = \frac{R_2 Cs + 1}{(R_1 + R_2)(Cs + 1)}$$

$$T.F = \frac{R_2}{R_1 + R_2} \cdot \frac{s + \frac{1}{R_2 C}}{s + \frac{1}{(R_1 + R_2)C}}$$

Let $T = R_2 C$ and $\beta = \frac{R_1 + R_2}{R_2}$, $\beta \gg 1$

$$T \cdot F = \frac{1}{\beta} \frac{s + \frac{1}{T}}{s + \frac{1}{\beta T}}$$

Pole-zero diagram

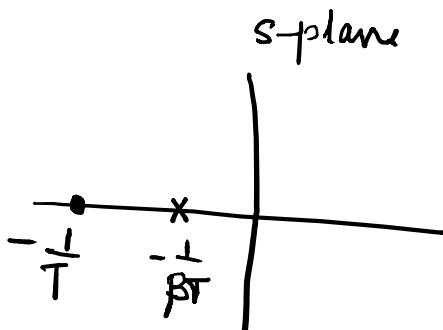

Effects of lag compensator

- It improves the steady state performance
- Bandwidth gets reduced
- System response becomes slower